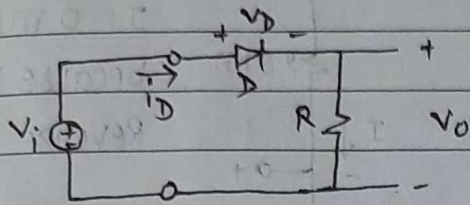


Q → For the circuit in Fig 4.3(a), sketch the transfer characteristic  $V_o$  versus  $V_i$ .




KVL  $-V_i + V_D + V_o = 0$   
 $V_o = V_i - V_D$  — (1)

graph of straight line!  $y = mx + c$   
 in equation (1) let  $V_D = 0.7$

so,  $V_o = V_i - 0.7$

Ans →

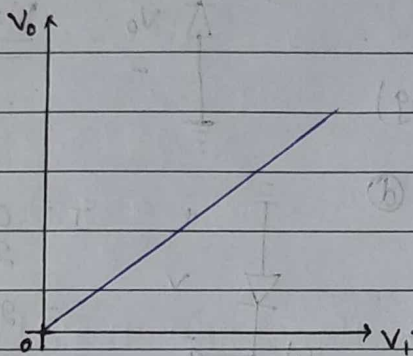

here  $c = -0.7$   
 $mx = V_i$



so, graph is straight line.

$$V_o = \begin{cases} 0 & V_i < 0.7 \\ V_i - 0.7 & V_i > 0.7 \end{cases}$$

Q → For the circuit in Fig 4.3(a), sketch the waveform of  $V_D$ .


Ans

$V_D = V_i - V_o$

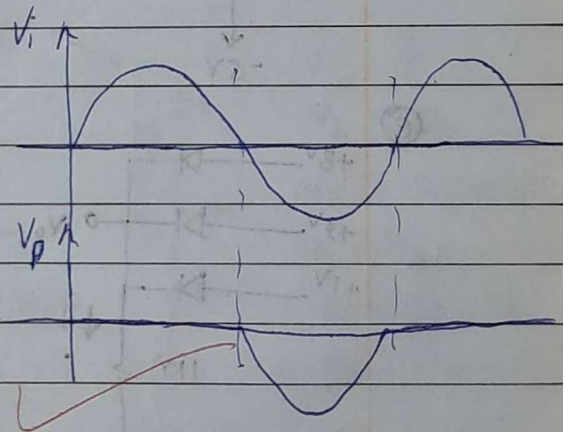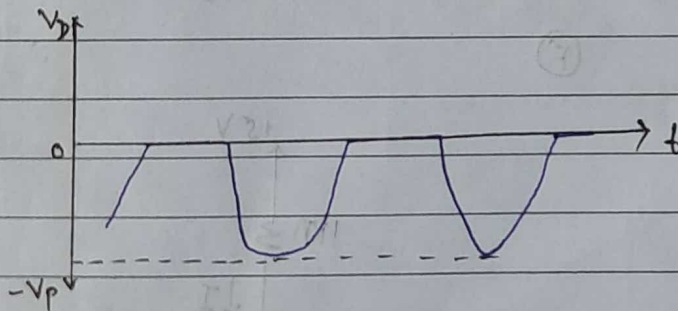

Q → in the circuit of Fig 4.3(a), let  $V_i$  have a Peak value of 10V and  $R = 5k\Omega$ . Find the Peak value of  $i_D$  and DC component of  $V_o$  (Hint, the average value of half-sine wave is  $(V_p/\pi)$ )

Soln

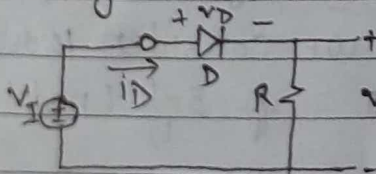

Given  $R = 5k\Omega$ ,  $V_i$  (Peak value) = 10V

$\therefore$  Peak value ( $i_D$ ) =  $\frac{10V}{5k\Omega} = 2mA$  Ans.


DC component of  $V_o = \frac{V_p}{\pi} = \frac{10}{\pi} = 3.18V$  Ans

Subject: \_\_\_\_\_


DATE: \_\_\_/\_\_\_/\_\_\_  
 MON TUE WED THU FRI SAT SUN  
 [ ] [ ] [ ] [ ] [ ] [ ] [ ]

(183) (4.4) Find the values of  $I$  &  $V$  in the circuit shown in Fig 4.4.


(a)

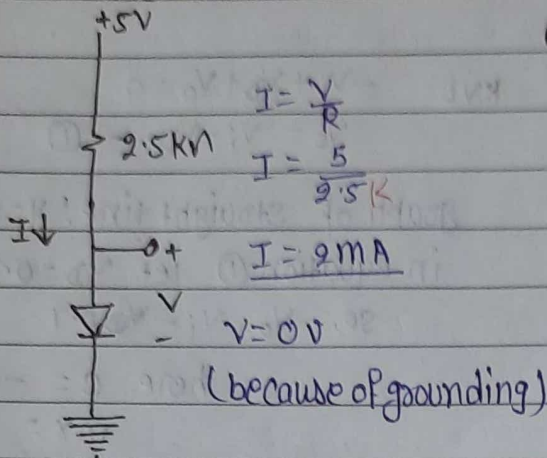


(b)

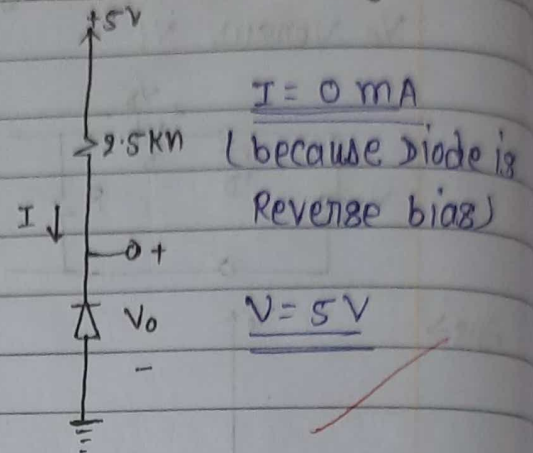


(c)

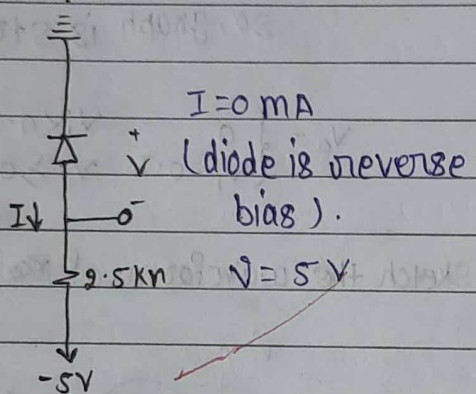

(d)

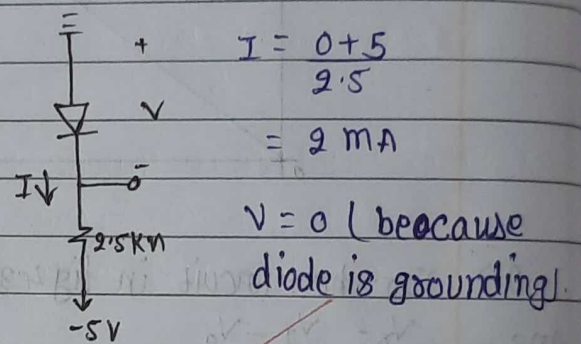


(e)

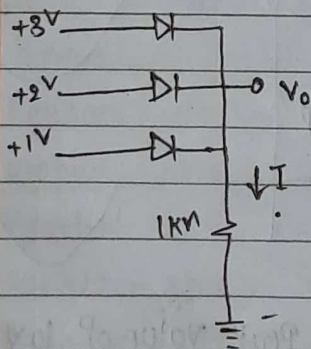

$V = 3V$  (logical or gate)  
 So, we consider higher value

$I = \frac{3V}{1k}$   
 $I = 3mA$

(f)

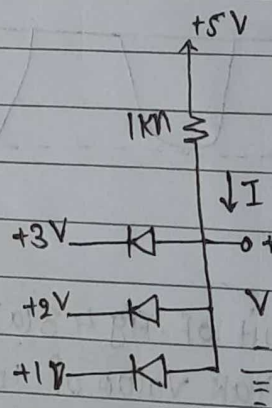


$V = 1V$  (logical and gate)  
 So we consider lower value.  
 $I = \frac{5-1}{1k}$  (node analysis)

$I = 4mA$



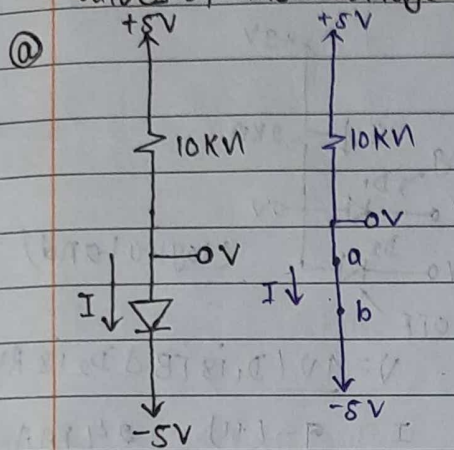Q42. For the circuits shown in Fig. P4.2 using ideal diodes. Find the values of the voltage & current indicated.




$$V_a > V_b \quad (5V > -5V)$$


so diode is forward biased.

$$I = \frac{5 - (-5)}{10} = 1 \text{ mA}$$

$$V = -5V$$

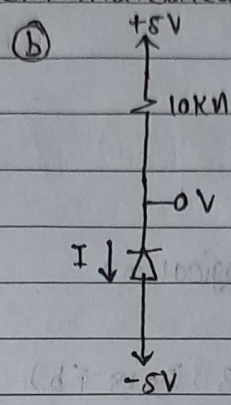

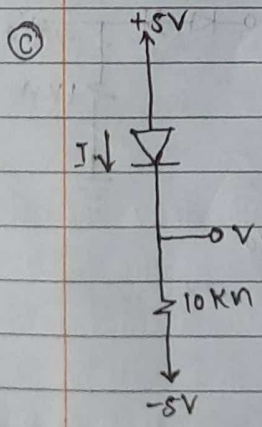$V_a > V_b$   
 $5V > -5V$   
 voltage of anode is less so diode behaves as open circuit.  
 so,  $I = 0 \text{ mA}$



$$V_a (\text{cathode}) > V_b (\text{anode})$$



so, diode behaves as short

circuit.

$$V = 5V$$

$$I = \frac{5 - (-5)}{10}$$

$$I = 1 \text{ mA}$$

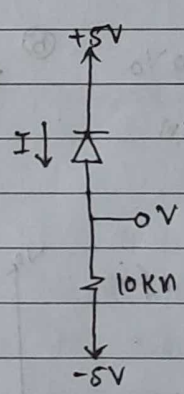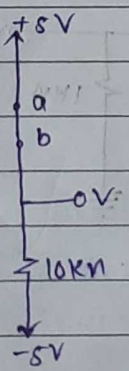

$V_b > V_a$   
 anode > cathode.  
 so, diode behave as a open circuit.

$$I = 0$$


$$-5 = -I \times 10k + V$$

$$-5 = 0 + V$$

$$V = -5V$$


Subject: \_\_\_\_\_

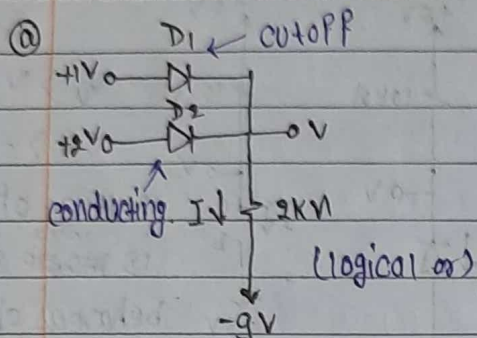4.3. For the circuit shown in fig P4.3 using ideal diodes, find the values of the labeled voltage & currents.



$$V = 9V \text{ (D}_1 \text{ is RB \& D}_2 \text{ is FB)}$$

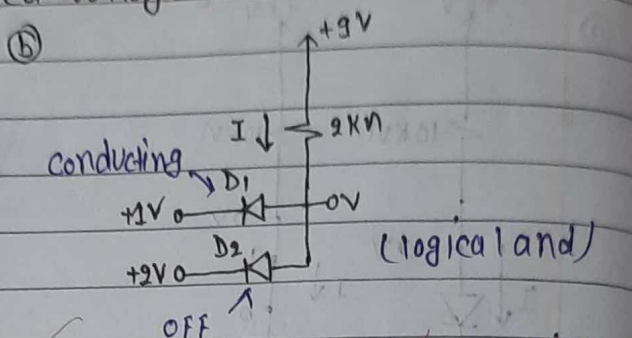
$$I = \frac{2 - (-9)}{2} = \frac{11}{2} = 5.5 \text{ mA}$$




$$V = 1V \text{ (D}_1 \text{ is FB \& D}_2 \text{ is RV)}$$

$$I = \frac{9 - (+1)}{2} = 4 \text{ mA}$$

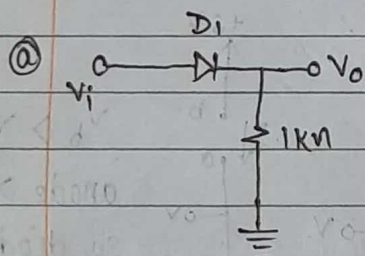4.4. in each of the ideal diode circuits shown in fig P4.4  $V_i$  is a 1-KHz, 5-V peak wave. sketch the waveform resulting at  $V_o$ , what are its positive and negative peak values?





Soln

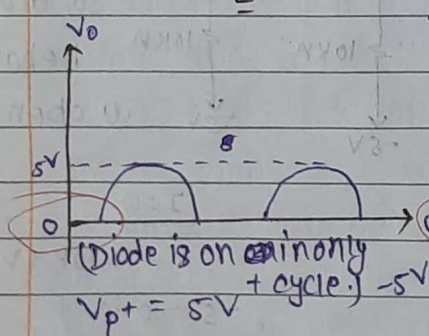


$$V_{p+} = 5V$$

$$V_{p-} = 0V$$

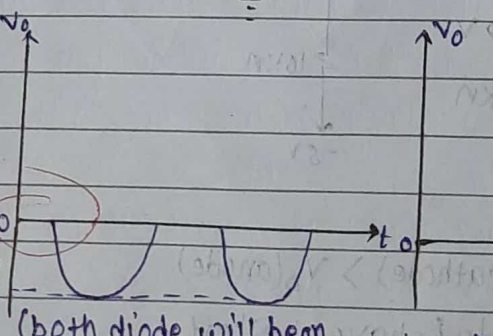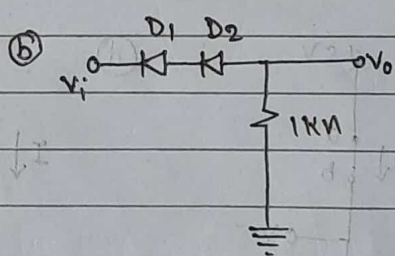


$$V_{p+} = 0V \text{ - cycle}$$


$$V_{p-} = -5V$$

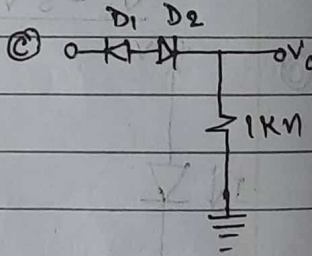


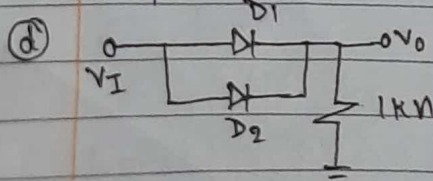
$V_o = 0V$   
D1 & D2 both are open circuit.




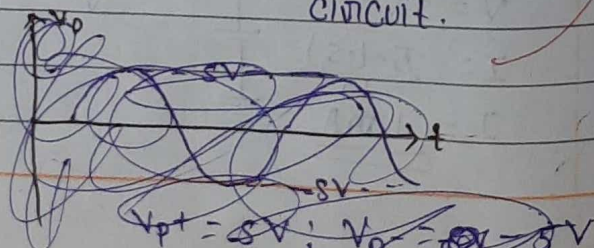
both D1 & D2 will be on on only positive half cycle input.







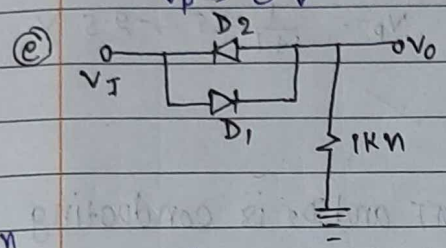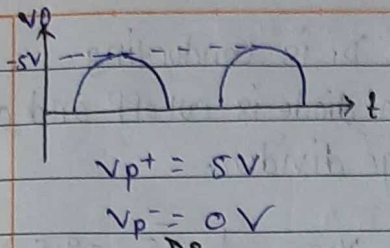

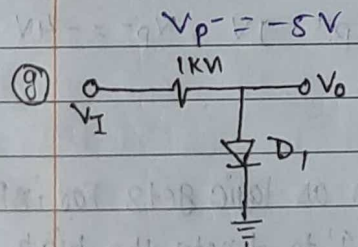
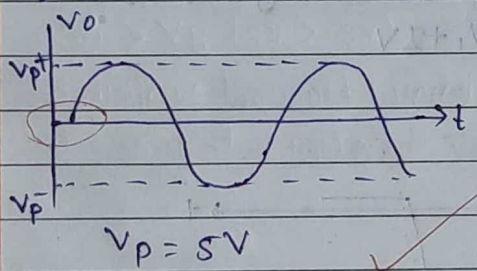
Sol<sup>n</sup>  
 $D_1$  conduct when  $v_i > 0$  &  
 $D_2$  —————  $v_i < 0$



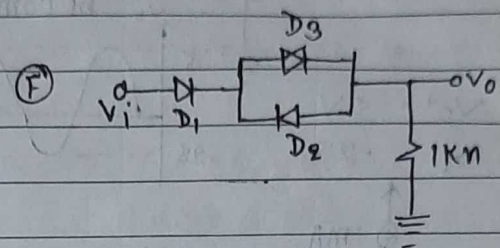
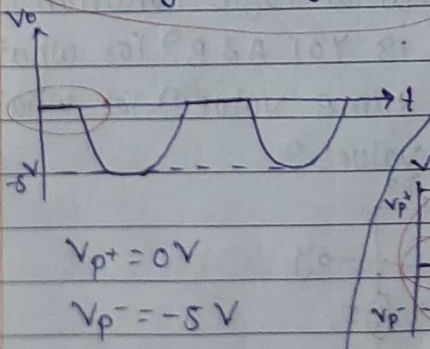
$D_1$  is on when  $v_i < 0V$   
 So, diode is conducting only  
 on (negative cycle).



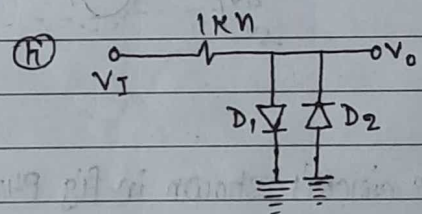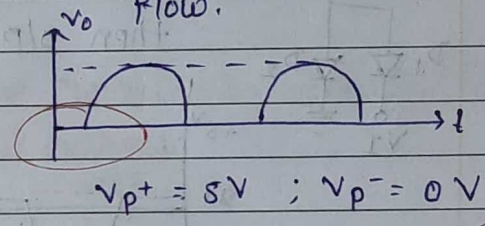Sol<sup>n</sup>  
 $D_1$  is cut off when  $v_i < 0$   
 $D_2$  is conducting only when  $v_i < 0$   
 so negative cycle current will not  
 flow.



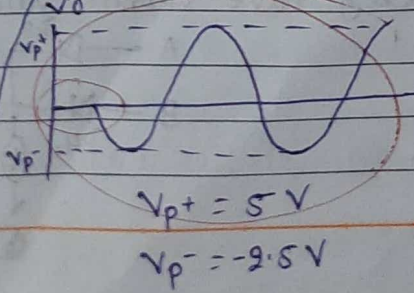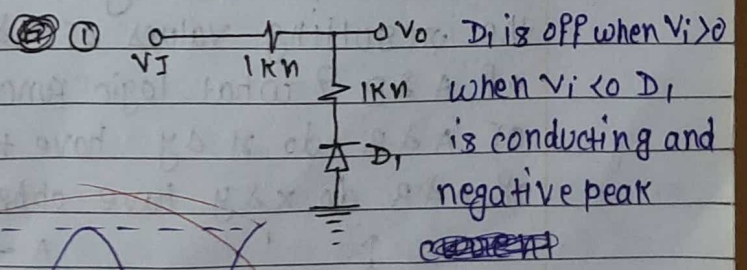
$v_O = 0V$  (both diode will be)  
 $D_1$  conducts when  $v_I > 0$  &  $D_2$   
 Conduct when  $v_I < 0$



$Voltage = \frac{1k\Omega}{1k\Omega + 1k\Omega} \times -5V$   
 $= -2.5V$   
 (voltage divider  
 rule)


Subject: \_\_\_\_\_

J.

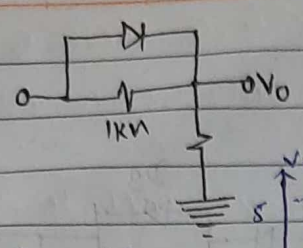


when  $V_i > 0$  then  $D_1$  is conducting  
 when  $V_i < 0$  then diode is cut off and circuit become a voltage divider.

$V_{p+} = 5V$   
 $V_{p-} = -2.5V$

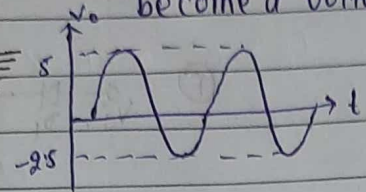


$V_{p-} = \frac{1}{1+1} \times 5 = -2.5V$

(K)

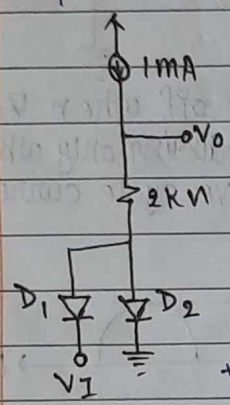


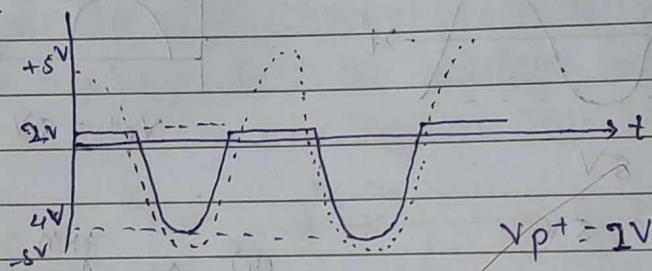
when  $V_i > 0$   $D_1$  is cut off and  $D_2$  is conducting the o/p becomes  $2V$ .  
 when  $V_i < 0$   $D_1$  is conducting and  $D_2$  will be off then o/p =  $V_i + 2V$



$V_{p+} = 2V, V_{p-} = -4V$

PP 282

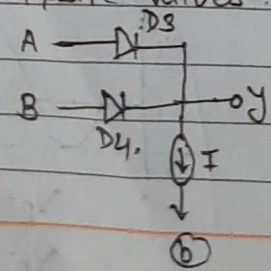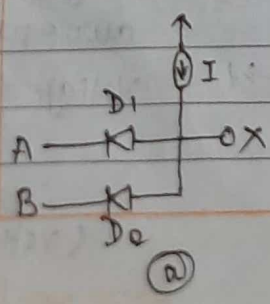Q4.6. The circuit shown in Fig P4.6 can function as logic gates. For input voltage that are either high or low using '1' to denote the high values and '0' to denote the low value, prepare a table with four columns including all possible input combinations and the resulting values of  $x$  &  $y$ . What logic function is  $x$  and of  $A$  &  $B$ ? What logic function is  $y$  of  $A$  &  $B$ ? For what value of  $A$  &  $B$  do  $x$  &  $y$  have the same value? For what values of  $A$  &  $B$  do  $x$  &  $y$  have opposite values?





A	B	X	Y
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

in Fig (a) x is connected to the output of AND gate with input A & B.



logic function of  $x = A \cdot B$  (AND gate)

in Fig (b) y is connected to the output of OR gate with input A & B

logical function of  $y = A + B$  (OR gate)

So, from the above table we can say that x & y have same value for  $A = B$  and they have opposite values for  $A \neq B$

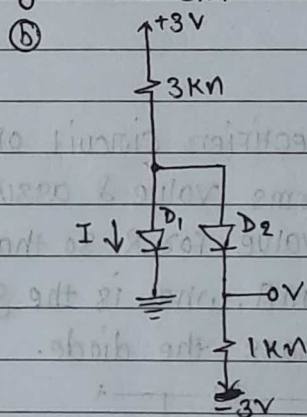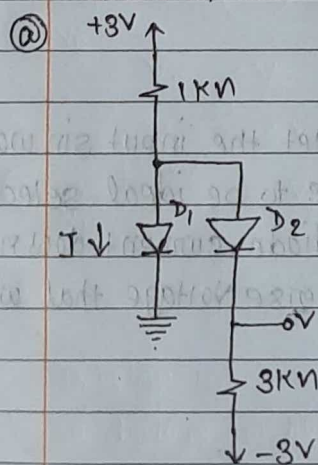P4.7 Assuming that the diode in the circuit P4.7 are ideal, Find the values of the labeled voltage & current.



sol<sup>n</sup> (a) if we assume both diode are conducting then  $V_0 = 0V$

$$I_{D2} = \frac{0 - (-3)}{3} = 1mA \quad I_{D1} = \frac{3 - 0}{1} = 3mA$$

A node equation at the common anode node yields a negative current in  $D_1$ , it means our assumption is wrong and  $D_1$  must be off, and  $D_2$  is on.

$$I_{D2} = \frac{3 - (-3)}{1+3} = \frac{3}{2} mA$$

$$I = 0$$

$$V = 1V$$

$$V = \frac{3}{2} \times 3 - 3 \Rightarrow 4.5 - 3 = 1.5V$$

Subject :

assume  $D_1$  &  $D_2$  both are conducting.

⑤  $I_3$  at  $3k\Omega$  Resistance  $= \frac{3-0}{3} = 1mA$

$I_1$  at  $1k\Omega$  resistance  $= \frac{0-(-3)}{1} = 3mA$

$I = I_3 - I_1$

$I = 1mA - 3mA$


$I = -2mA$  Ans

So,  $V = 0$  Ans

983

E4.9

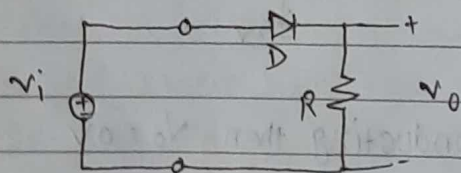For the rectifier circuit of Fig 4.3 (a), let the input sin wave have  $120V_{rms}$  value & assume the diode to be ideal. select a suitable value for  $R$  so that the Peak diode current does not exceed  $40mA$ , what is the greatest reverse voltage that will appear across the diode.



$R \geq \frac{120\sqrt{2}}{40}$  ~~28.2 kΩ~~

$R \geq 4.24 k\Omega$

The largest reverse voltage appearing across the diode is equal to the Peak input voltage  $120\sqrt{2} = 169.7 V$